

Control of Inverters

PulseWidth Modulation and Space Vector PWM



Prof. Ashwin M Khambadkonne

email: eleamk@nus.edu.sg

Dept. of ECE, National University of Singapore


DC to DC conversion and PWM

Step-down Power converter

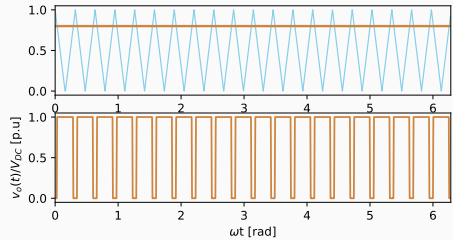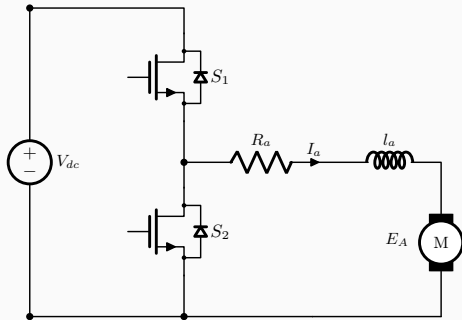

Sketch the armature current waveform.

Step-down Power converter for 4 Quadrant

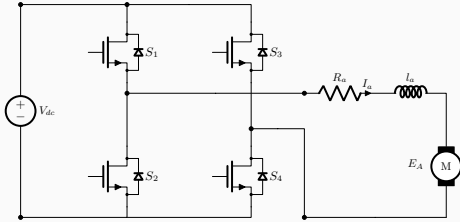


The average value of v_a is

$$\bar{v}_a = \frac{1}{T_s} \int_0^{T_s} v_a(t) dt$$

$$\bar{v}_a = \frac{V_{dc} T_{on}}{T_s} - \frac{V_{dc}(T_s - T_{on})}{T_s}$$

$$\bar{v}_a = V_{dc}[2D - 1]$$

$$\text{where } D = \frac{T_{on}}{T_s}$$

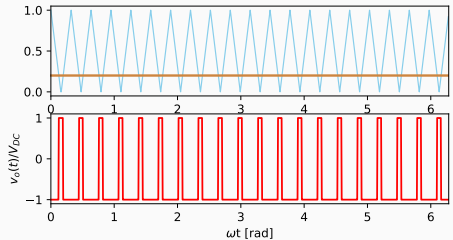


The output voltage v_a is a pulsewidth modulated waveform. It has a period of T_s and

$$v_a = V_{dc} \quad 0 < t < T_{on}$$

$$v_a = -V_{dc} \quad T_{on} < t < T_s$$


DC to AC converter

Producing AC from a DC source

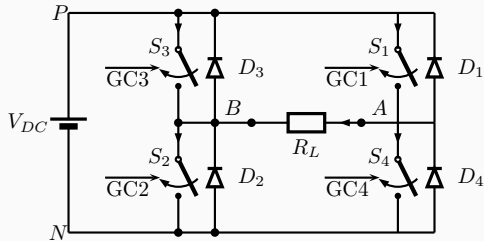


- Sketch the voltage waveform v_{AB} for few complete AC cycles
- Sketch the current waveform i_{AB} for the corresponding voltage cycles?
- Sketch the waveform for $\overline{GC1}$ and $\overline{GC3}$ for corresponding voltage cycles?

3 Phase Inverter Circuit

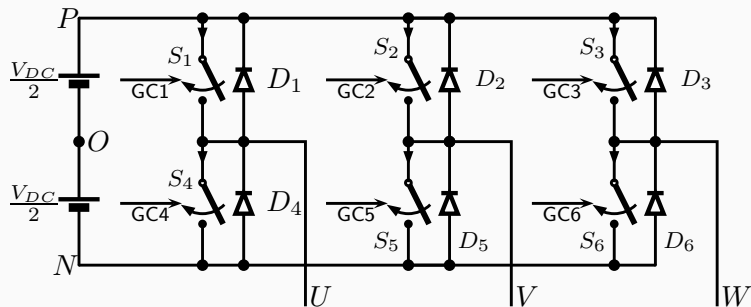


Space Vectors associated with the switching states

S	$v_s(S)$ Polar	$v_s(S)$ rectangular
100	$\frac{2}{3} V_{DC} e^{j0}$	-
110	$\frac{2}{3} V_{dc} e^{j\frac{\pi}{3}}$	-
010	$\frac{2}{3} V_{dc} e^{j\frac{2\pi}{3}}$	-
011	$\frac{2}{3} V_{dc} e^{j\pi}$	-
001	$\frac{2}{3} V_{dc} e^{j\frac{4\pi}{3}}$	-
101	$\frac{2}{3} V_{dc} e^{j\frac{5\pi}{3}}$	-
111	0	$0 + j0$
000	0	$0 + j0$

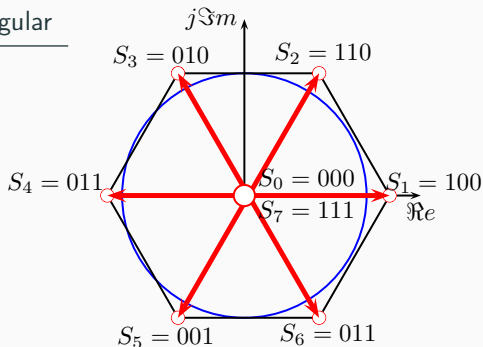


Space Vectors during Six-Step Operation

S	$v_s(S)$ Polar	$v_s(S)$ rectangular
100	$\frac{2}{3} V_{DC} e^{j0}$	-
110	$\frac{2}{3} V_{dc} e^{j\frac{\pi}{3}}$	-
010	$\frac{2}{3} V_{dc} e^{j\frac{2\pi}{3}}$	-
011	$\frac{2}{3} V_{dc} e^{j\pi}$	-
001	$\frac{2}{3} V_{dc} e^{j\frac{4\pi}{3}}$	-
101	$\frac{2}{3} V_{dc} e^{j\frac{5\pi}{3}}$	-
111	0	$0 + j0$
000	0	$0 + j0$

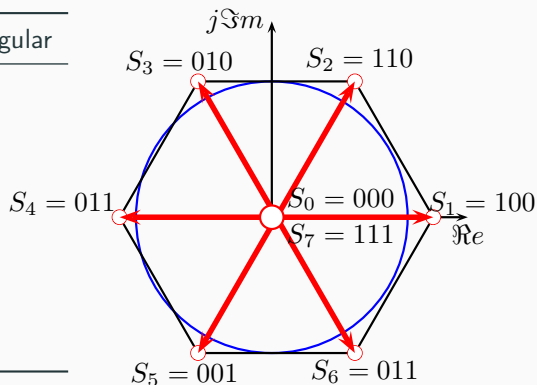


Six-Step Operation

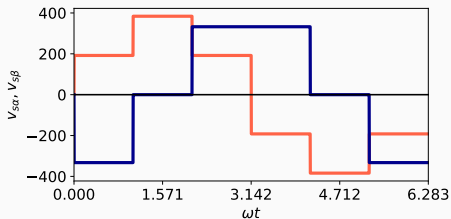

Switching each state for $1/6$ of fundamental period produces a six-step operation

switching state	(S_U, S_V, S_W)
S_1	1 0 0
S_2	1 1 0
S_3	0 1 0
S_4	0 1 1
S_5	0 0 1
S_6	1 0 1

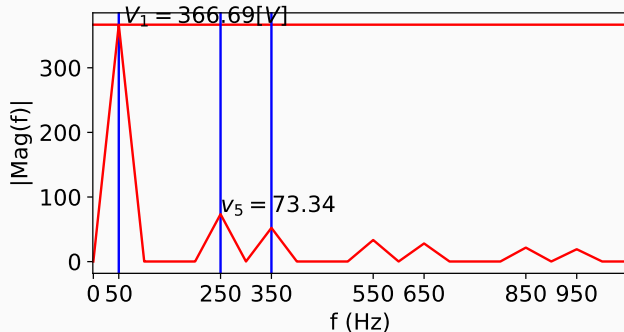Six-Step Operation: Low Frequency Harmonics present



By Fourier Analysis,
peak value of
fundamental component
of Six-Step Wave is

$$\hat{V}_{\text{six-step}} = \frac{2}{\pi} V_{DC}$$

Since $V_{DC} = 576 \text{ [V]}$,
we get

Low freq,. harmonics

- 5,7,11,13th harmonics are present
- Large filter needed to remove them

$$\hat{V}_{\text{six-step}} = 366.69 \text{ [V]}$$



Fourier Series of phase voltage

Fourier Series Quasi Square Wave

$$f(\omega t) = \sum_{h=1,3,5..}^{\infty} \frac{4M}{h\pi} \cos(h\alpha) \sin(h\omega t) \quad V_{sa}$$

For square wave $\alpha = 0$, hence
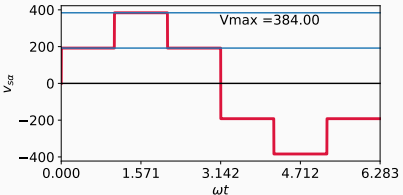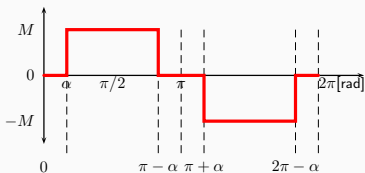
$$f(\omega t) = \sum_{h=1,3,5..}^{\infty} \frac{4M}{h\pi} \sin(h\omega t)$$




Phase voltage can be expressed of 2 waveforms

- A quasi square wave with $M = \frac{V_{DC}}{3}$ and $\alpha = \frac{\pi}{3}$
- and A Square wave with $M = \frac{V_{DC}}{3}$

Hence the fundamental component ($n = 1$) of the phase voltage during Six-step operation can be written as

Fourier Series of phase voltage

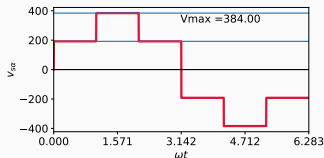

Phase voltage can be expressed of 2 waveforms

- A quasi square wave with $M = \frac{V_{DC}}{3}$ and $\alpha = \frac{\pi}{3}$
- and A Square wave with $M = \frac{V_{DC}}{3}$

Hence the fundamental component ($n = 1$) of the phase voltage during Six-step operation can be written as

$$V_{1,\text{six-step}} = \frac{4}{\pi} \left(\frac{V_{DC}}{3} \right) \cos \left(\frac{\pi}{3} \right) + \frac{4}{\pi} \left(\frac{V_{DC}}{3} \right) \quad (1)$$

$$V_{1,\text{six-step}} = \frac{4}{\pi} \left(\frac{V_{DC}}{3} \right) \left[1 + \cos \left(\frac{\pi}{3} \right) \right] \quad (2)$$

$$V_{1,\text{six-step}} = \frac{4}{\pi} \left(\frac{V_{DC}}{3} \right) \left[1 + \frac{1}{2} \right] \quad (3)$$

$$V_{1,\text{six-step}} = \frac{2}{\pi} V_{DC} \quad (4)$$

The maximum Fundamental Frequency voltage an Inverter can produce

Maximum Fundamental Frequency voltage


- During Six-step operation maximum voltage is produced by inverter
- The fundamental frequency voltage for six-step operation is found using fourier series
- Fundamental frequency can be changed by changing the fundamental period ($f_1 = 50\text{Hz}$ is rated in Singapore)

The peak value of fundamental component of phase voltage during six-step is


$$\hat{V}_{1,\text{six-step}} = \frac{2}{\pi} V_{DC} \quad (5)$$

Sine Wave Pulse Width Modulation (SWPWM)

3 Phase Inverter Circuit

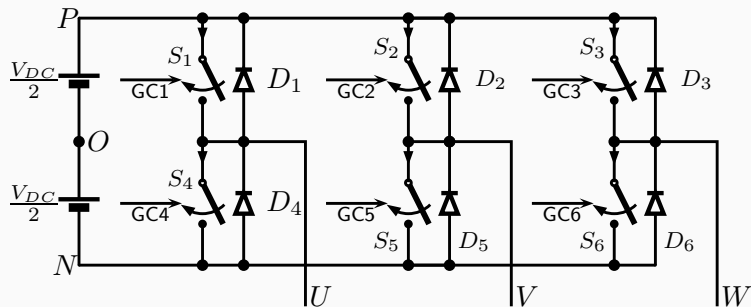


Principle of Pulsewidth Modulation (PWM)

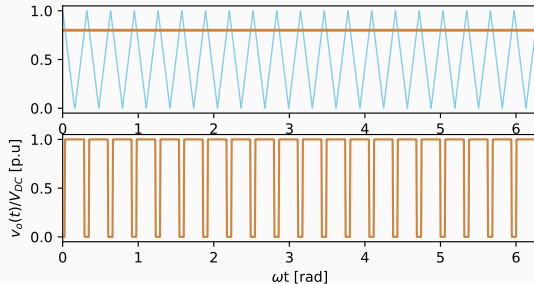


- Use a high frequency triangular carrier wave
- Compare it with desired reference wave
- When
if($V_{ref} > V_{carrier}$)**then:** $S = 1.0$, **else:** $S = 0$
- Output is a high frequency switched waveform - peak value - constant
- Pusewidth of the waveform varies as the value of $V_{ref}(t)$

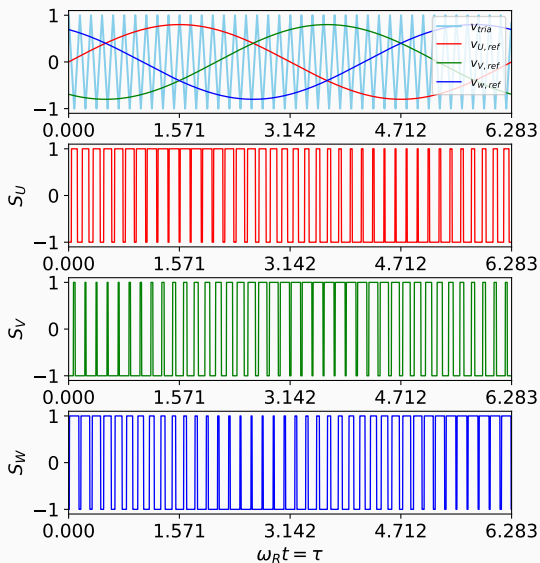3 phase Sinewave Puslewidth Modulation (SWPWM)




- Use a high frequency triangular carrier wave
- Compare it with 3 phase sinewave
- When $\text{if}(V_{ref} > V_{carrier}) \text{then: } S = 1.0, \text{ else: } S = 0$
- Logic Output used for switching
 $S = 1 \text{ then Top Switch on}$
- $S = 0 \text{ then bottom Switch on}$
- Inverter produces 3 phase voltages

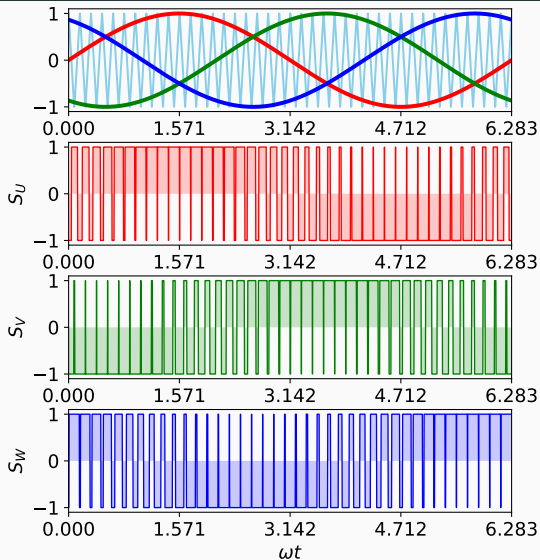3 phase Sinewave Puslewidth Modulation Averages per cycle (SWPWM)




- Use a high frequency triangular carrier wave
- Compare it with 3 phase sinewave
- When $\text{if}(V_{ref} > V_{carrier}) \text{ then } S = 1.0, \text{ else } S = 0$
- Logic Output used for switching
 $S = 1$ then Top Switch on
 $S = 0$ then bottom Switch on
- Inverter produces 3 phase voltages

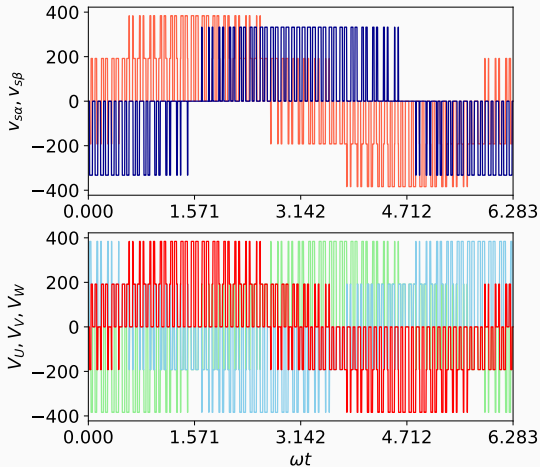3 phase Sinewave Pusewidth Modulation (SWPWM)



- Top Graph - Space Vector Voltages
- Bottom Graph - 3 phase Voltages

Why use PWM?

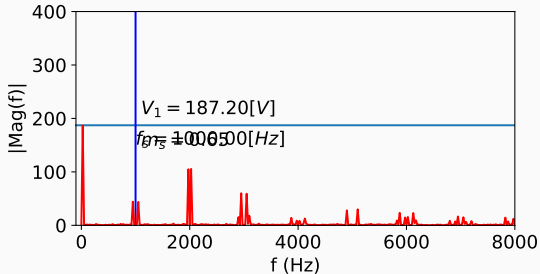

- The fundamental and harmonics get separated in frequency domain
- By using higher carrier frequency, dominant harmonics get pushed to right
- It becomes easier to filter higher harmonics with smaller filter size
- filter cut-off is $\omega_c = \frac{1}{\sqrt{LC}}$

$$m_s = \frac{\text{Peak value of reference}}{\text{Peak value of carrier}}$$



$$= \frac{\hat{V}_{ref}}{\hat{V}_{carrier}}$$

General Definition of Modulation Index

For any type of PWM, Modulation index m_i is defined as

$$m_i = \frac{\text{peak value of fundamental voltage produced by the PWM}}{\text{peak value of fundamental voltage during six-step}} = \frac{\hat{V}_{PWM}}{\frac{2}{\pi} V_{DC}} \quad (6)$$

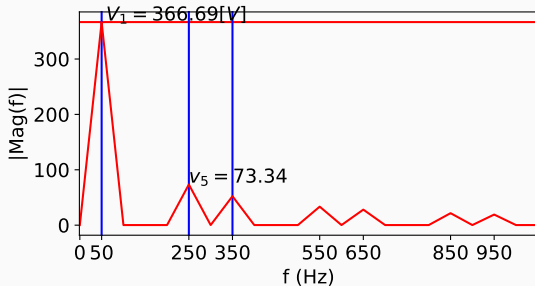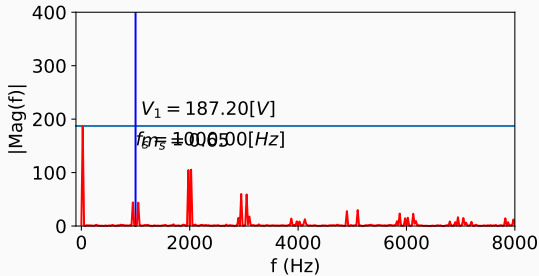SWPWM does not allow us to get the maximum voltage



- for $V_{DC} = 576[V]$
- max Voltage with SWPWM
 $= V_{DC}/2 = 288[V]$
- max possible fundamental
 Voltage with Six Step
 $\frac{2}{\pi} V_{DC} = 366.69[V]$

maximum modulation index in SWPWM


$$\hat{m}_{i, \text{SWPWM}} = \frac{\frac{V_{DC}}{2}}{\frac{2}{\pi} V_{DC}} \quad (7)$$

$$= \frac{\pi}{4} \quad (8)$$


$$= 0.785 \quad (9)$$

IM currents for six step operation

at no load

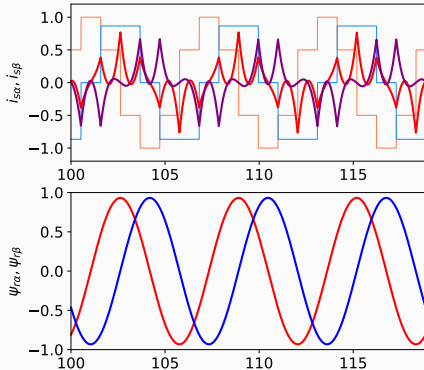

with loading

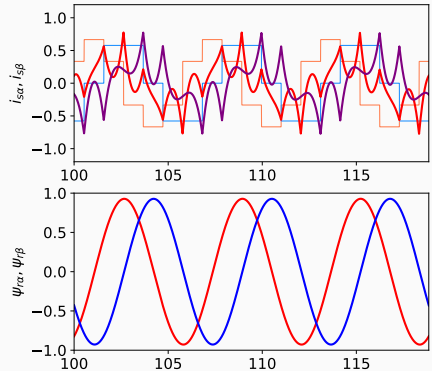


The current are non-sinusoidal with lower order harmonics. However, the flux is sinusoidal. This is because the impedance of the motor acts as low pass filter

SWPWM cannot utilize the full voltage capability of the Inverter


SWPWM cannot produce the maximum voltage

- Maximum Fundamental voltage the SWPWM can produce is only $\frac{V_{DC}}{2}$
- Maximum Capability of 3 phase inverter is $\hat{V}_{1,\text{six-step}} = \frac{2}{\pi} V_{DC}$
- Hence SWPWM utilizes only 78% of the total voltage capability of the 3 phase inverter

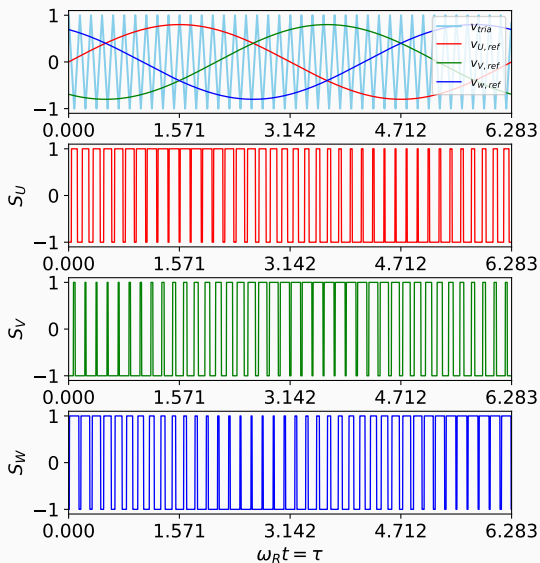3 phase Sinewave Puslewidth Modulation (SWPWM)



Functional Circuit for PWM

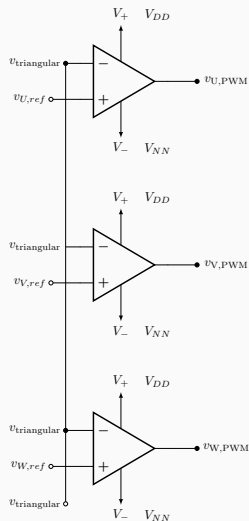

3 phase Sinewave Puslewidth Modulation (SWPWM) Results

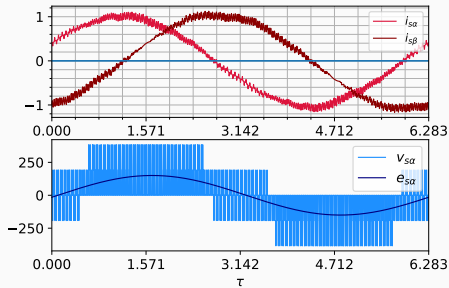


Figure 1: Motor currents space vector component (top) and α Stator voltage and back-emf (bottom)

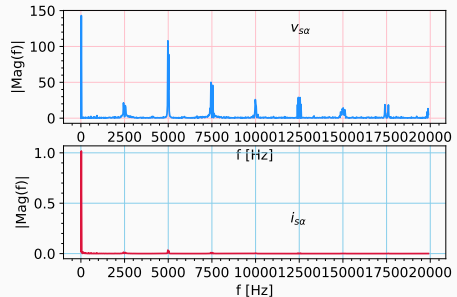


Figure 2: Spectrums of voltage (top) and current (bottom)

Motor impedance acts as filter

Though the applied stator voltage has high distortion due to PWM, the motor current harmonics are negligible as the motor impedance acts as low pass filter

Comparison of stator currents SWPWM vs Six-Step

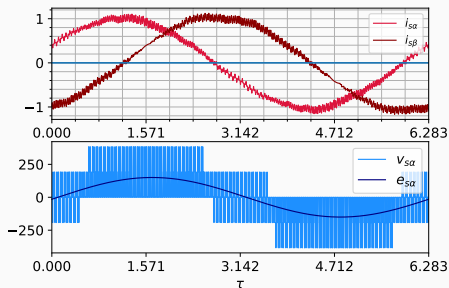


Figure 3: Motor currents space vector component (top) and α Stator voltage and back-emf (bottom)

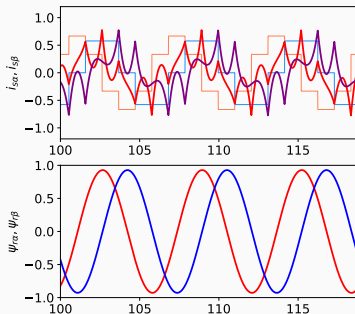


Figure 4: motor current due to Six-step operation

PWM controlled inverter better

Current Distortion and Torque ripple is lower in PWM fed motors

Increasing switching frequency lowers distortion

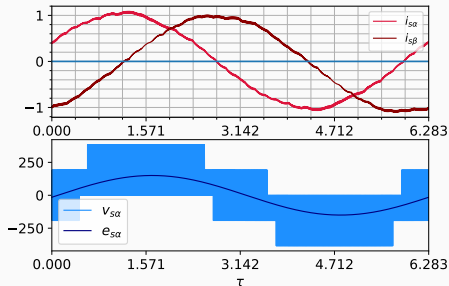


Figure 5: Motor currents space vector component (top) and α Stator voltage and back-emf (bottom)

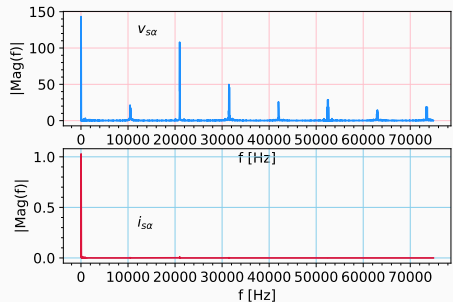


Figure 6: Spectrums of voltage (top) and current (bottom)

Motor impedance acts as filter

Higher the switching frequency, lower the distortion, so many researchers want to increase the switching frequency....but

Increasing switching frequency causes higher iron losses

Usually Ferromagnetic Iron used in core.
Manufacture give loss density [W/kg] as

$$w_{Fe} = \underbrace{k_h f B^\alpha}_{\text{Hysteresis Loss}} + \underbrace{k_e f^2 B^2}_{\text{Eddy current Loss}} + \underbrace{k_a f^{3/2} B^{3/2}}_{\text{anomalous Loss}}$$

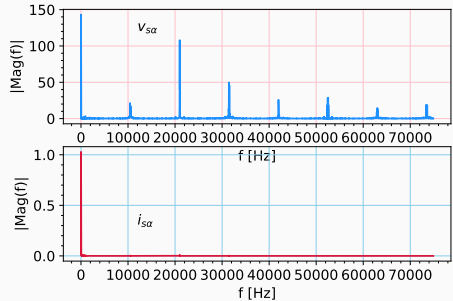



Figure 7: Spectrums of voltage (top) and current (bottom)

Motor impedance acts as filter

Higher the switching frequency, causes higher losses in iron of the motor....**The Irons losses are proportional to square of frequency**


Power Electronic System used in Drives

Typical Single Quadrant AC drives

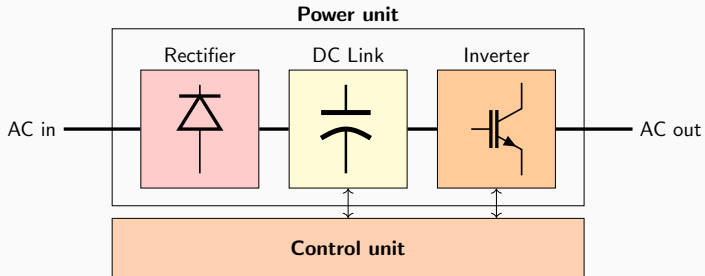


- AC input is converted into DC using 3 phase diode rectifier
- DC Link capacitor acts as energy storage
- DC Voltage is converted to 3 phase PWM AC voltage by 3 phase inverter

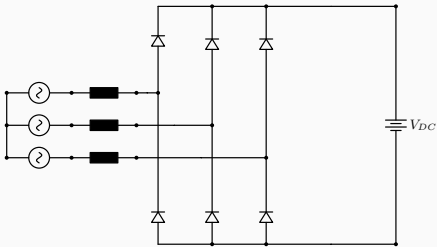
Three phase Diode Rectifier: Distorted line current



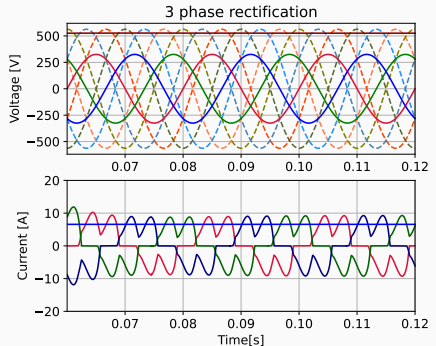
Diode in turns on when forward biased and turn-off when diode current goes to zero



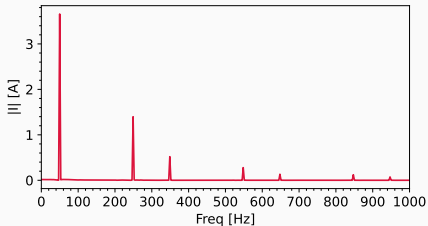Three phase Diode Rectifier: Line current spectrum




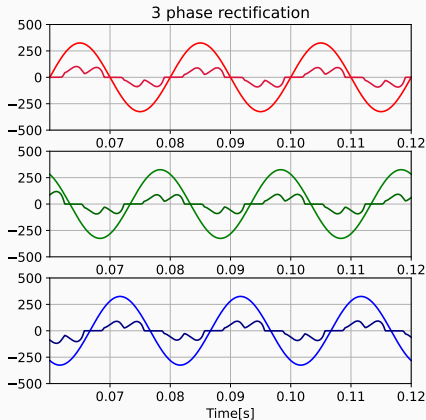contains lower order odd harmonics
5,7,11,13...(3rd does not flow in a star
connected 3 phase)




Individual phase currents

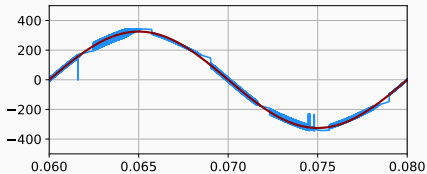Three phase Diode Rectifier: Distortion at PCC voltage due to distorted line currents




$$v_{pcc} = v_g - L_1 \frac{di_g}{dt}$$

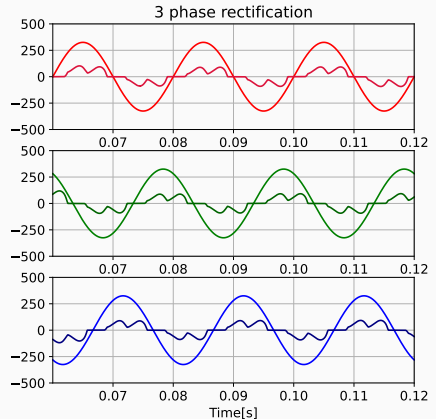Any other device connected at PCC sees distorted voltage, due to the non-sinusoidal voltage drop $L_1 \frac{di_g}{dt}$ caused due to distorted currents



Individual phase currents


4 Quadrant AC drives

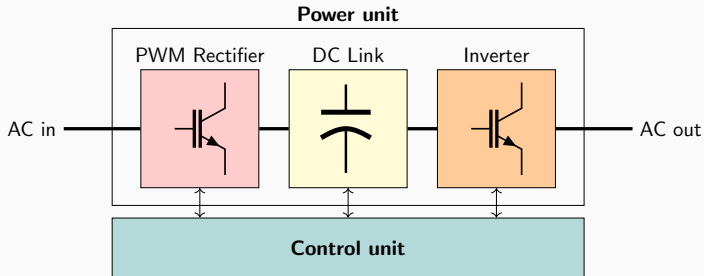

- AC input is converted into DC using 3 PWM rectifier, it gives unity power factor on the grid side
- DC Link capacitor acts as energy storage
- DC Voltage is converted to 3 phase PWM AC voltage by 3 phase inverter

Space Vector Modulation (for knowledge only)


3 phase Voltage Source Inverter Circuit

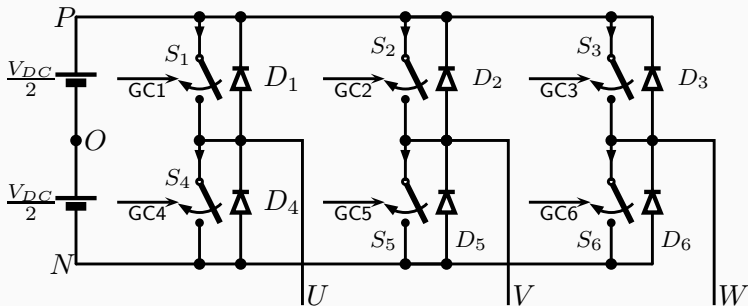

$$\vec{v}_s(S) = \frac{2}{3} \left(V_{U,N} + e^{j\frac{2\pi}{3}} V_{V,N} + e^{j\frac{4\pi}{3}} V_{W,N} \right) \quad (10)$$


$$\vec{v}_s(S) = \frac{2}{3} V_{DC} \left(S_U + e^{j\frac{2\pi}{3}} S_V + e^{j\frac{4\pi}{3}} S_W \right) \quad (11)$$

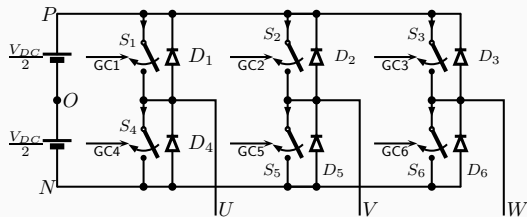Space Vectors and Switching state of 3p VSI




switching state (S_U, S_V, S_W)

S_0	0 0 0
S_1	1 0 0
S_2	1 1 0
S_3	0 1 0
S_4	0 1 1
S_5	0 0 1
S_6	1 0 1
S_7	1 1 1

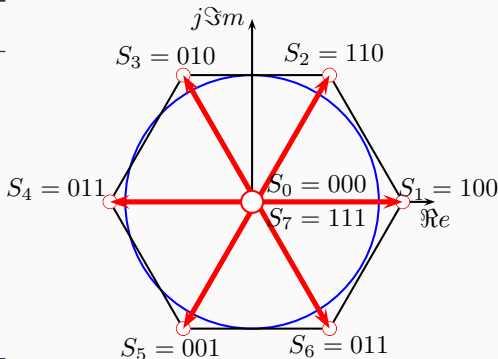


Sectors of Space Vector Switching Plane

Sector	angle
Sec(0)	$0 \rightarrow \frac{\pi}{3}$
Sec(1)	$\frac{\pi}{3} \rightarrow \frac{2\pi}{3}$
Sec(2)	$\frac{2\pi}{3} \rightarrow \pi$
Sec(3)	$\pi \rightarrow \frac{4\pi}{3}$
Sec(4)	$\frac{4\pi}{3} \rightarrow \frac{5\pi}{3}$
Sec(5)	$\frac{5\pi}{3} \rightarrow 2\pi$

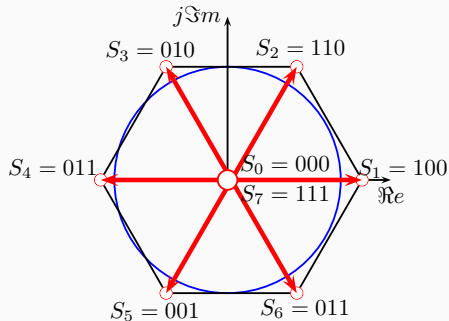

Space Vectors associated with the switching states

S	$v_s(S)$ Polar	$v_s(S)$ rectangular
100	$\frac{2}{3} V_{DC} e^{j0}$	-
110	$\frac{2}{3} V_{dc} e^{j\frac{\pi}{3}}$	-
010	$\frac{2}{3} V_{dc} e^{j\frac{2\pi}{3}}$	-
011	$\frac{2}{3} V_{dc} e^{j\pi}$	-
001	$\frac{2}{3} V_{dc} e^{j\frac{4\pi}{3}}$	-
101	$\frac{2}{3} V_{dc} e^{j\frac{5\pi}{3}}$	-
111	0	$0 + j0$
000	0	$0 + j0$

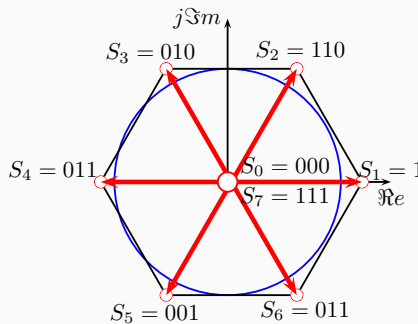

Definition of Space vector Modulation

Definition

The volt-second produced by the reference voltage space vector \vec{v}_s^* in period T_s should be equal to the voltage-seconds produced by the switching state vectors.

In a given sector, with vertices \vec{v}_r , \vec{v}_l and zero vectors v_0, v_7 , we can write the volt-sec balance as

$$\vec{v}_s^* T_s = \vec{v}_r t_a + \vec{v}_l t_b + v_0 t_0 \quad (12)$$

and

$$T_s = t_r + t_l + t_0$$

Space Vector Modulation SVM or SVPWM

$$\vec{v}_s^* T_s = \vec{v}_r t_r + \vec{v}_l t_l + v_0 t_0 \quad (13)$$

$$\vec{v}_s^* T_s = \vec{v}_r t_r + \vec{v}_l t_l \quad (14)$$


$$T_s = t_r + t_l + t_0 \quad (15)$$

$$v_{s\beta}^* = \vec{v}_l \sin\left(\frac{\pi}{3}\right) t_l \quad (16)$$

$$\therefore t_l = \frac{v_{s\beta}^*}{|\vec{v}_l| \sin\left(\frac{\pi}{3}\right)} T_s \quad (17)$$

$$\frac{t_l}{T_s} = \frac{v_{s\beta}^*}{\frac{2}{3} V_{DC} \sin\left(\frac{\pi}{3}\right)} \quad (18)$$

$$\frac{t_l}{T_s} = \frac{|\vec{v}^*| \sin(\gamma)}{\frac{2}{3} V_{DC} \sin\left(\frac{\pi}{3}\right)} \quad (19)$$

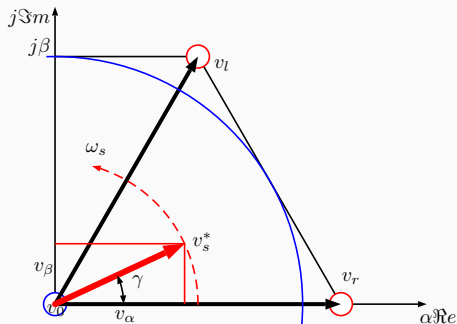

SVM switching Times t_r

$$\vec{v}_s^* T_s = \vec{v}_r t_r + \vec{v}_l t_l + v_0 t_0 \quad (20)$$


$$\vec{v}_s^* T_s = \vec{v}_r t_r + \vec{v}_l t_l \quad (21)$$

$$T_s = t_r + t_l + t_0 \quad (22)$$

$$v_{s\alpha}^* = \vec{v}_r t_r + \vec{v}_l \cos\left(\frac{\pi}{3}\right) t_l \quad (23)$$

substituting t_l in above equation we get


$$t_r = \frac{|\vec{v}_s^*|}{\frac{2}{3} V_{DC}} \frac{\sin\left(\frac{\pi}{3} - \gamma\right)}{\sin\left(\frac{\pi}{3}\right)} T_s \quad (24)$$

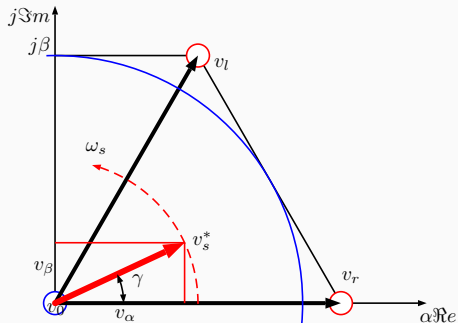

Switching Sequence of SVM in Sector 0

on times	$t_0/2$	t_r	t_l	$t_0/2$	$t_0/2$	t_l	t_r	$t_0/2$
vector	\vec{V}_0	\vec{V}_r	\vec{V}_l	\vec{V}_7	\vec{V}_7	\vec{V}_l	\vec{V}_r	\vec{V}_0
Sec(0)	S_0	S_1	S_2	S_7	S_7	S_2	S_1	S_0
State	(0,0,0)	(1,0,0)	(1,1,0)	(1,1,1)	(1,1,1)	(1,1,0)	(1,0,0)	(0,0,0)

Switching Sequence in sector 0

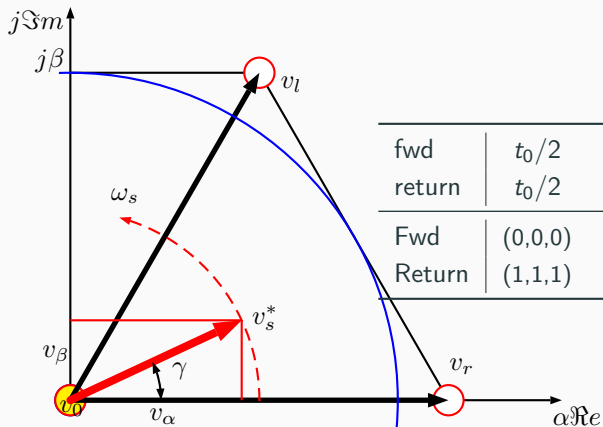


fwd	$t_0/2$	t_r	t_l	$t_0/2$
return	$t_0/2$	t_l	t_r	$t_0/2$
Fwd	(0,0,0)	(1,0,0)	(1,1,0)	(1,1,1)
Return	(1,1,1)	(1,1,0)	(1,0,0)	(0,0,0)

For the sequence in sector zero sketch $v_{s\alpha}, v_{s\beta}$

fwd	$t_0/2$	t_r	t_l	$t_0/2$
return	$t_0/2$	t_l	t_r	$t_0/2$
Fwd	(0,0,0)	(1,0,0)	(1,1,0)	(1,1,1)
Return	(1,1,1)	(1,1,0)	(1,0,0)	(0,0,0)

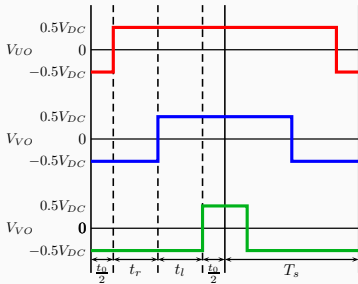
Phase Voltages with respect to DC link Mid-point



sector 0 sequence

fwd	$t_0/2$	t_r	t_l	$t_0/2$
return	$t_0/2$	t_l	t_r	$t_0/2$
Fwd	(0,0,0)	(1,0,0)	(1,1,0)	(1,1,1)
Return	(1,1,1)	(1,1,0)	(1,0,0)	(0,0,0)

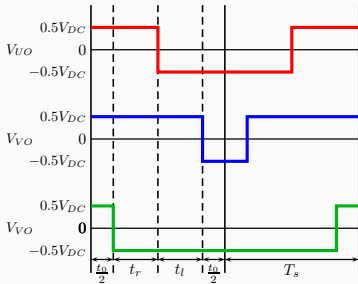
Phase Voltages with respect to DC link Mid-point



sector 1 sequence


Fwd	$t_0/2$	t_r	t_l	$t_0/2$
return	$t_0/2$	t_r	t_l	$t_0/2$
Fwd	(1,1,1)	(1,1,0)	(0,1,0)	(0,0,0)
Return	(0,0,0)	(0,1,0)	(1,1,0)	(1,1,1)

Switching Sequence in sector 1

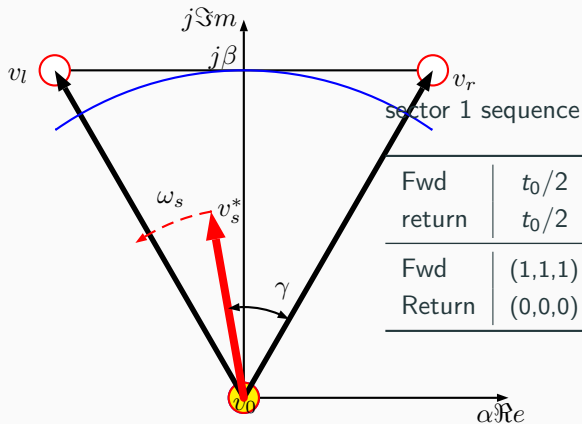


Fwd	$t_0/2$	t_r	t_l	$t_0/2$
return	$t_0/2$	t_r	t_l	$t_0/2$
Fwd	(1,1,1)	(1,1,0)	(0,1,0)	(0,0,0)
Return	(0,0,0)	(0,1,0)	(1,1,0)	(1,1,1)

Space Vector Modulation voltages

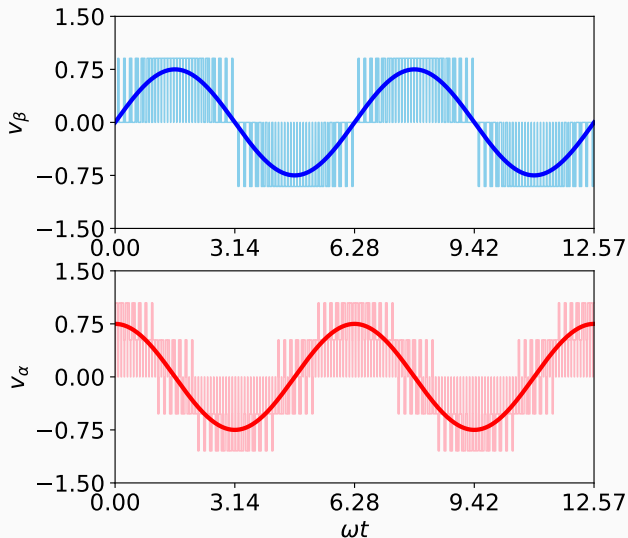


- Modulation index
 $m_i = 0.75$
- Switching frequency
 $f_s = 39 * 50\text{kHz}$
- Fundamental Frequency
 $f_1 = 50\text{Hz}$
- Normalization base
 $V_{1,\text{six-step}} = \frac{2}{\pi} V_{DC}$
- Normalized peak value of
 $V_{s\alpha} = \frac{\frac{2}{3} V_{DC}}{\frac{2}{\pi} V_{DC}} = \frac{\pi}{3}$

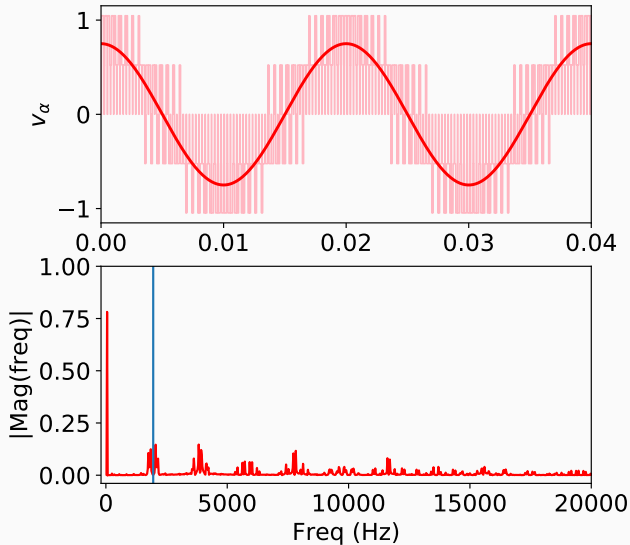Space Vector Modulation phase voltage and Spectra



- Modulation index
 $m_i = 0.75$
- Switching frequency
 $f_s = 39 * 50\text{kHz}$
- Fundamental Frequency
 $f_1 = 50\text{Hz}$
- Normalization base
 $V_{1,\text{six-step}} = \frac{2}{\pi} V_{DC}$
- Normalized peak value of
 $V_{s\alpha} = \frac{\frac{2}{3} V_{DC}}{\frac{2}{\pi} V_{DC}} = \frac{\pi}{3}$

SVM switching times in Sector 0

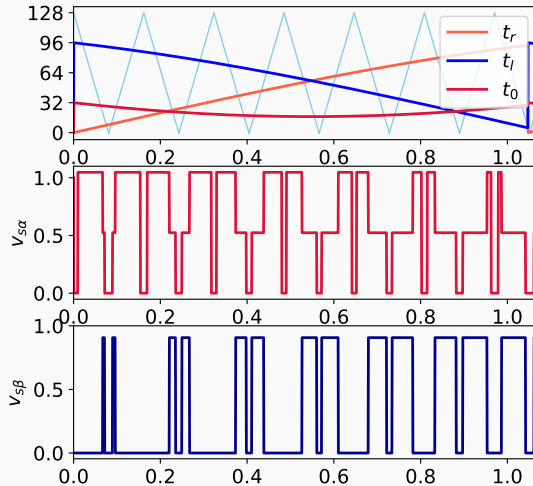

- 128 bit counters is $2f_s$
- t_r , t_l and t_0 change with angle/time
- $v_{s\alpha}$ has PWM output

Maximum fundamental frequency Voltage produced by SVM

SVM


Maximum Fundamental Frequency component

Length of space vector = $\frac{2}{3} V_{DC}$
when blue circle touches hexagon,
magnitude of reference voltage will be

$$\hat{V}_{1,svm} = \frac{2}{3} V_{DC} \cos\left(\frac{\pi}{6}\right) \quad (25)$$

$$\hat{V}_{1,svm} = \frac{2}{3} \frac{\sqrt{3}}{2} V_{DC} \quad (26)$$
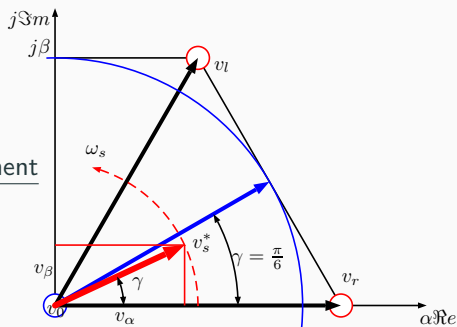
$$\hat{V}_{1,SVM} = 0.577 V_{DC} \quad (27)$$



- Red dotted circle describes the trajectory of fundamental voltage
- Maximum fundamental voltage trajectory is given by blue circle
- At $\gamma = \frac{\pi}{6}$, $t_0 = 0$ when blue circle touches the hexagon

Maximum Modulation Index for SVM

The maximum modulation index using SVM is

$$\hat{m}_{i,svm} = \frac{\text{maximum fundamental voltage by SVM}}{\text{maximum fundamental voltage during six-step}} \quad (28)$$


$$\hat{m}_{i,svm} = \frac{0.577 V_{DC}}{\frac{2}{\pi} V_{DC}} \quad (29)$$

$$\hat{m}_{i,svm} = 0.906 \quad (30)$$

SVM utilizes voltage capacity better than SWPWM


Hence SVM utilizes 90.6% of the installed voltage capability

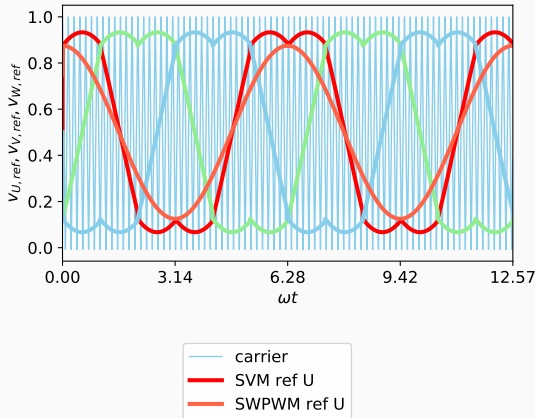Why SVM produces more fundamental voltage than SWPWM



- The sinewave reference is used in SWPWM
- But, SVM produces a reference that has
- 3rd harmonic component add to fundamental
- Triplen ($\times 3$) harmonics do not flow in 3 phase circuits.


Implementing PWM in Practice

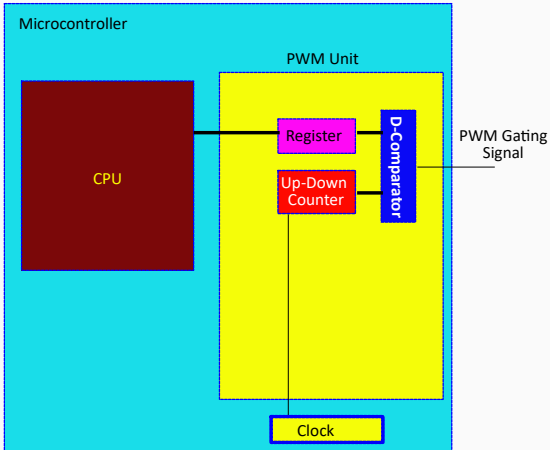


- Every Microcontroller has a count-n-compare unit
- Consists of an Up-down counter
- A set of registers (3 for 3 phase needed)
- A comparator
- A buffered output to drive the gate of Inverter

[illegible]

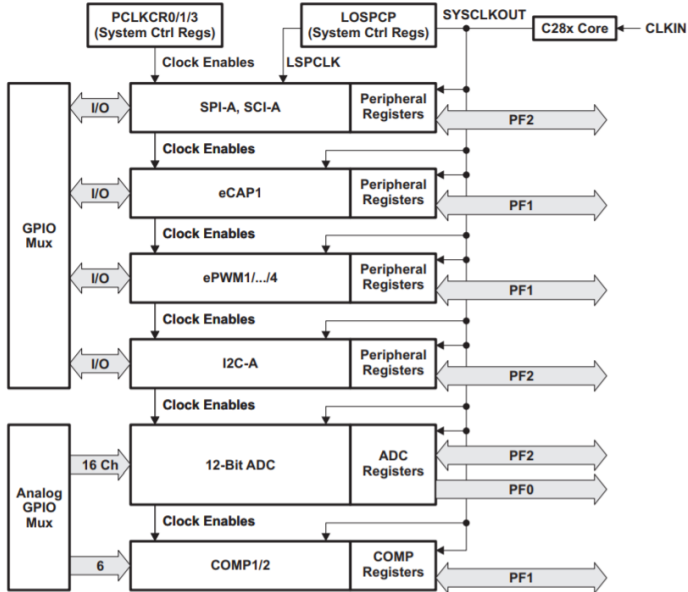Example of Practical Microcontroller output unit




Implementing PWM in Practice

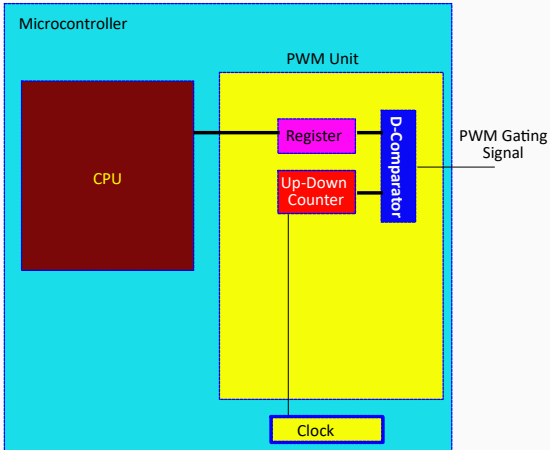

- Compute t_r , t_l and t_0
- Depending on position of reference voltage vector,
- compute t_U , t_V and t_W
- Put the values in Registers
- Compare with counter
- D-Comparator output to gate drive unit

Implementing PWM in Practice

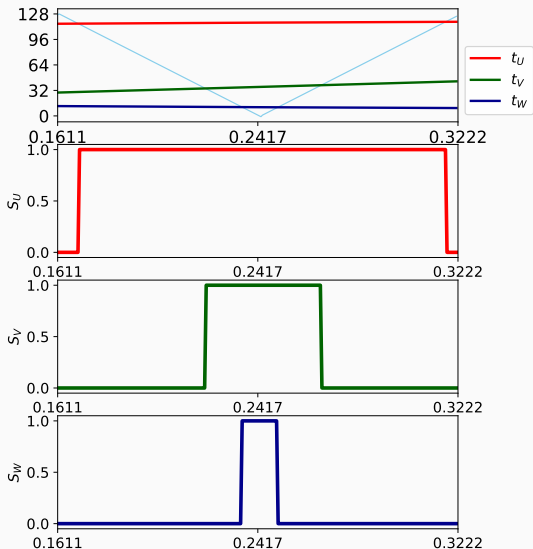


- Compute t_r , t_l and t_0
- Depending on position of reference voltage vector,
- compute t_U , t_V and t_W
- Put the values in Registers
- Compare with counter
- D-Comparator output to gate drive unit

Current Control of Inverters




- For AC drives we need current control
- VSI is essentially a controlled voltage source
- 3 phase AC output can be generated using PWM methods (SWPWM, SVM)
- How do we get current control

Non-linear Current Control

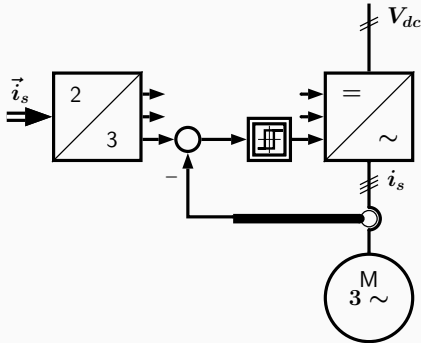


- Actual Current is compared with reference current
- A non-linear (Bang-Bang controller) is used to produce switching states
- Hysteresis is added in practices and that decides the switching frequency
- The Switching frequency is not constant
- Suited for low power application with fast dynamic
- Basic Idea: Analog control paradigm using Comparators

Non-linear Current Control

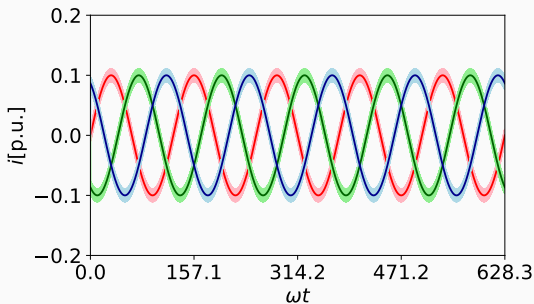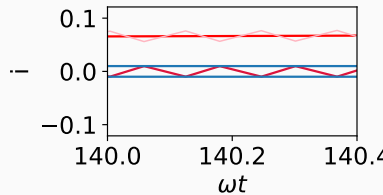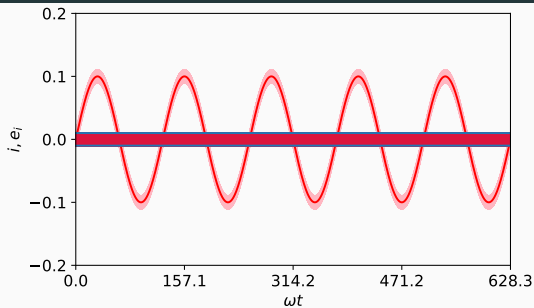

Linear Current Control: PI Control in Field Coordinates

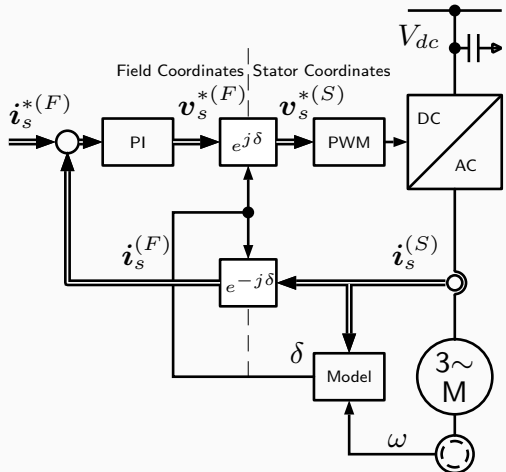- In field coordinates, we see currents as DC (zero frequency)
- This is due to coordinate transform in a synchronous frequency reference frame
- It is called Field-oriented Current control as the reference frame is oriented along rotor flux space vector



Non-linear Current Control vs Linear Current Control

Non-linear Current Control

- + Fast Response
- + Parameter dependency is less
- + Good for analog implementation
- Switching frequency keeps varying
- Switching frequency depends on parameters
- Suited for low power applications
- Many implement Non-linear control digitally, so they lose the advantage of analog

Linear Current Control

- + Switching frequency can be decided
- + Control performance + PWM performance can be chosen
- + Digital Implementation is easier
- Parameter dependent performance (can be tuned)
- Transient Response depends on controller characteristics
- Digital Implementation: Transient response

Power Electronic devices used in VSC for drives

