




2Nov23

Thursday, November 2, 2023 6:00 PM

Today's class


- { 1. How to get variable voltage variable frequency
- 2. Inverters, DC2Ac converter
- 3. PWM principle.
- 4. Sincwave PWM
- 5. Spacevector Modulation - principle.
- 6. Devices used in voltage source converters

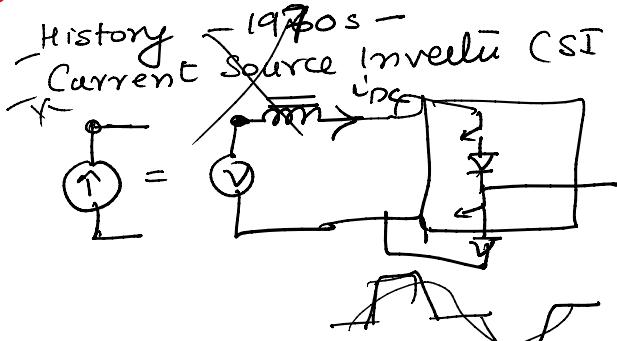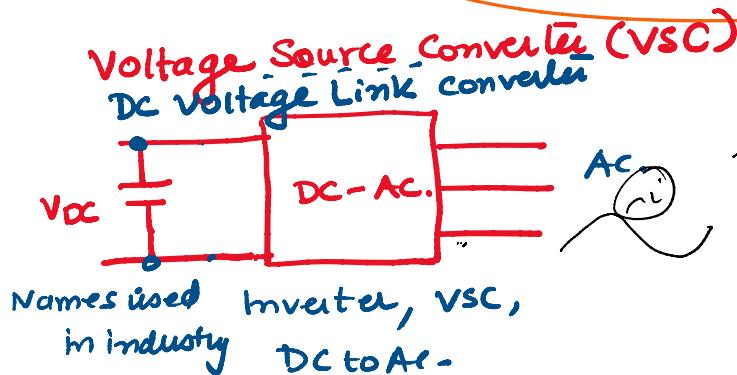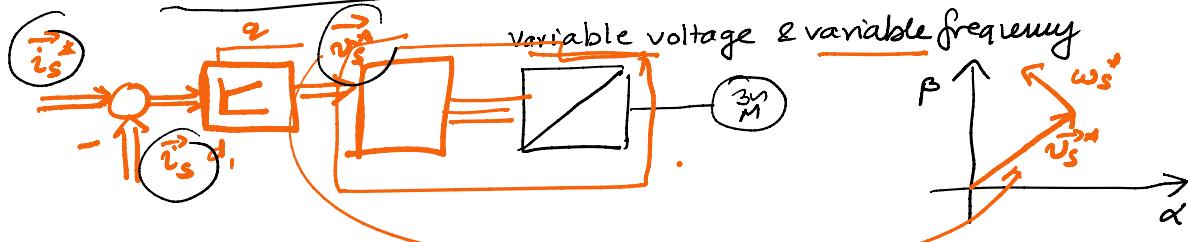Problem solving & How to study for EEE37003



Requirement

$$\phi \text{ const.} \quad \frac{|U_{S1}|}{|\omega_S|} = \text{const.}$$

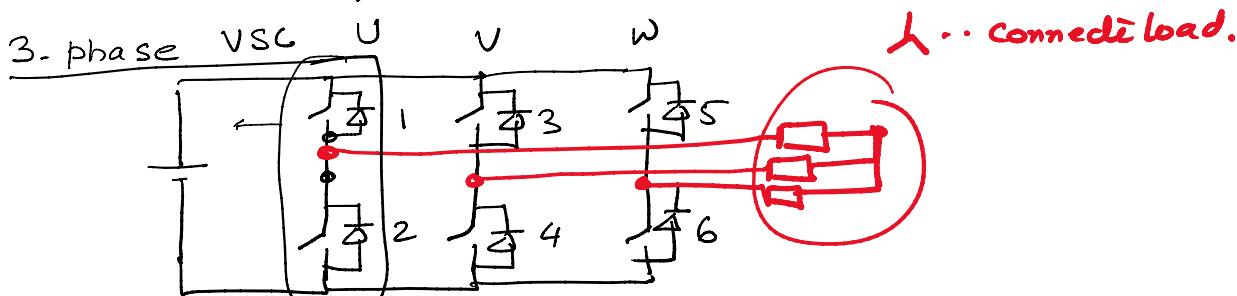


phase leg U has 2 states

$$SU=1, Q_1=1, Q_2=0, SU=0, Q_1=0, Q_2=1$$


Total number of states

$$(\text{state})^{\text{phase}} = 2^3 = 8$$

	SU	SV	SW
1	1	0	0
2	1	1	0

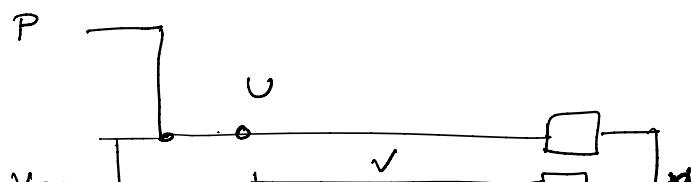

	1	1	0
2	1	1	0
3	0	1	0
4	0	1	1
5	0	0	1
6	1	0	1

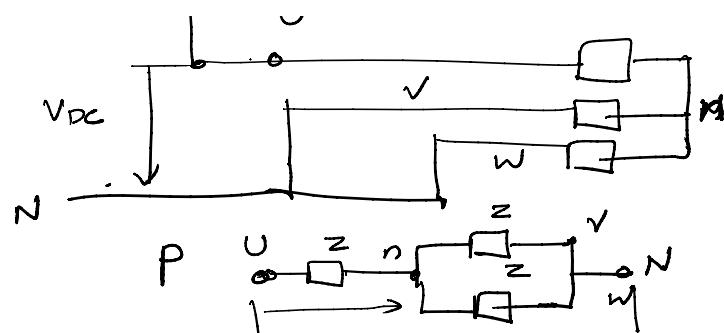


$$V_{UN} = \frac{2}{3} V_{DC} \quad V_{VN} = -\frac{1}{3} V_{DC} = V_{WN}.$$



8 1 1 1 000


$$\boxed{V_\alpha} = \boxed{V_{UN}} \quad \text{phase voltage?}$$
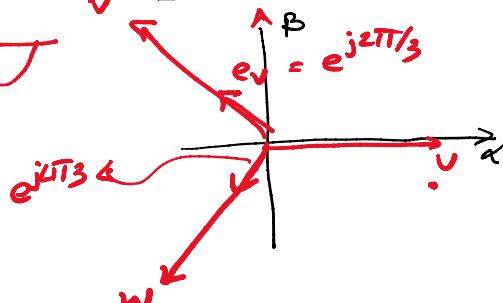
$$\boxed{V_{vn}} = \underline{\hspace{10cm}}$$




$$V_{\alpha-\beta} = T \cdot \begin{bmatrix} V_{UN} \\ V_{VN} \\ V_{WN} \end{bmatrix}$$
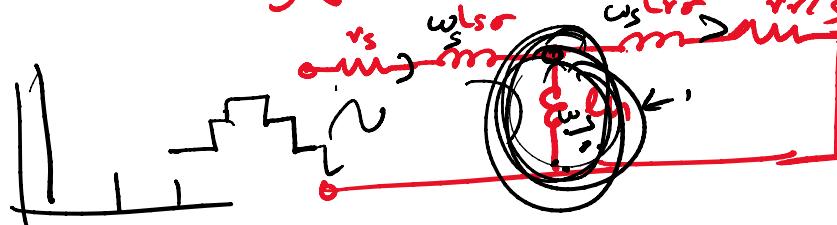
$$V_\alpha + jV_\beta = \frac{2}{3} (V_{UN} + (-\frac{1}{2} + j\frac{\sqrt{3}}{2})V_{VN} + (-\frac{1}{2} - j\frac{\sqrt{3}}{2})V_{WN})$$





$$L_s = L_h + L_{s0}$$


mutual flux

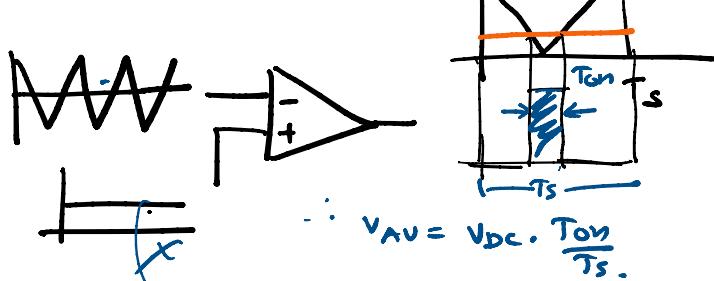

MC

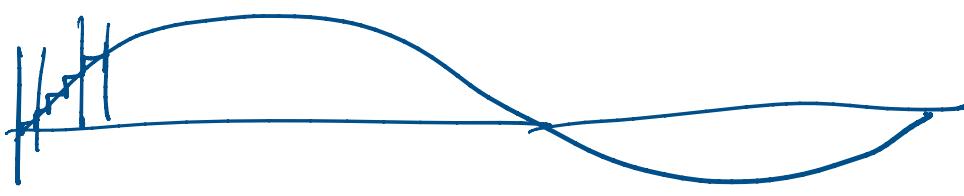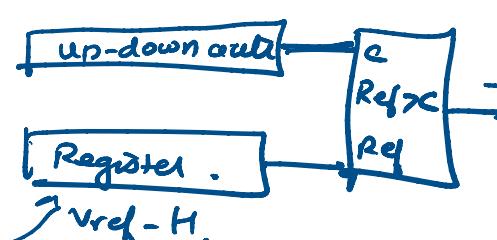

t < t_{tot} + t_{refl}, Caten Machinee

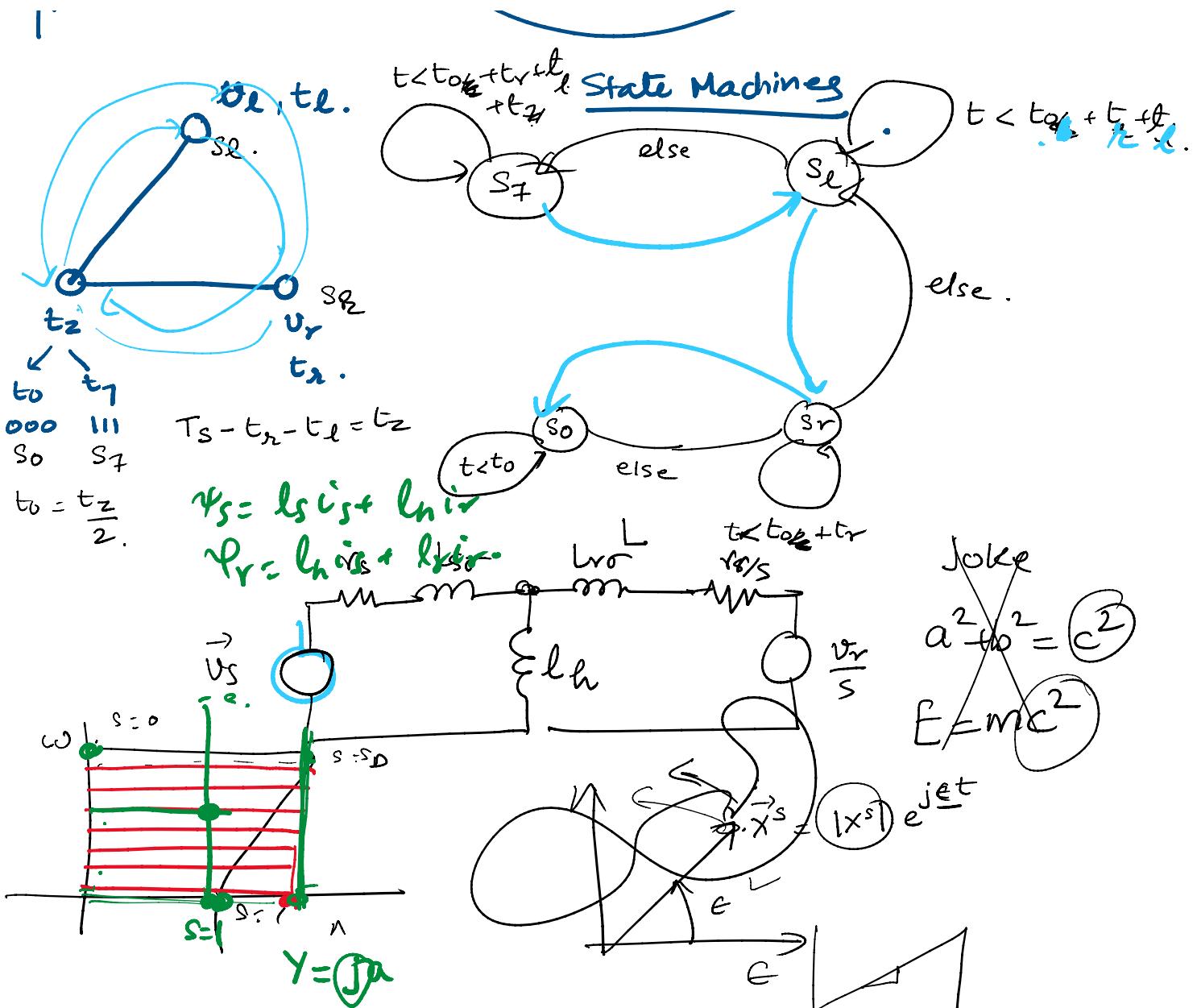

Faraday's

$$v_i = \frac{d^4 s}{dt} = j\omega \cancel{4_s}$$

$$|U_1| = \cancel{2\pi} \cdot 4s.$$

$$\frac{|v_i|}{|\psi_i|} = k \rho_s.$$

$$j\omega s \Psi_s e^{j\theta} = \sin\theta + j\cos\theta.$$

$$e^{j\theta} = \sin\theta + j\cos\theta =$$


$$x(t) = \sin \underline{\theta} \underline{t}$$

$$\omega t = \theta .$$

$$y = \frac{dx(t)}{dt} = \cos \omega t \cdot \omega.$$

$$\underline{Y} = \frac{1}{dt}$$
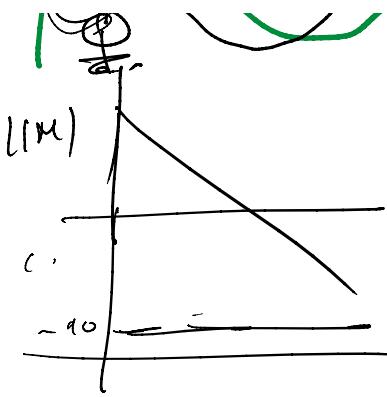
$$\int x(t) dt = -\frac{\cos \omega t}{\omega}$$



- ① An IM ... is running steady state -- no load --
I disconnect the stator from supply

